

Schematic for node 1

- OSC 1 : 4.9512 MHz] Crystal oscillators
- OSC 2 : 16.0000 MHz
- R1 : 4.7k Ω
- R2 : 10k Ω
- R3 : 10k Ω
- R4 : 1.0k Ω
- R5 : 10k Ω
- RG : 18k Ω
- RF : 22k Ω

All capacitors are 100nF

